

## Audio Volume Control

By Saul Ushen


14 Sept 2018

### Introduction:

We built a volume control circuit for audio applications.
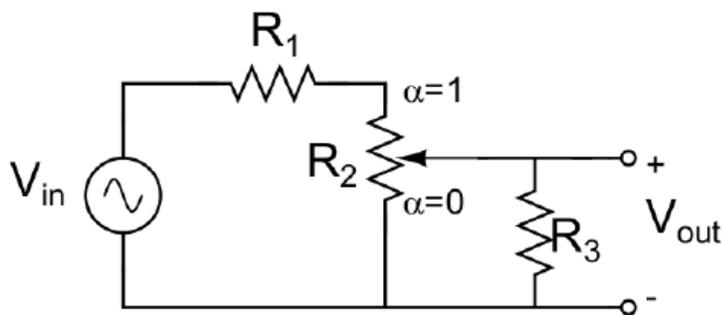
### Design/measurements:

The circuit design was provided. The main principle of operation is that the circuit acts as a voltage divider. When we turn the knob, the voltage output will increase or decrease, hence the volume of the song will do the same.




We measured the voltage output, which can be assumed to be proportional to audible volume.

Measurements were taken at alpha values of 0-1 in increments of about 0.1. We varied alpha by turning the potentiometer. We expect  $V_{out}/V_{in}$  to follow a voltage divider equation.

### Results:

Here are our results for the measurements. We see that the output voltage increases with alpha, as expected. When the knob is maxed out, we get a value of  $V_{out}/V_{in}$  of about 0.73. Also, we did a test drive of our volume circuit. We did this by using a computer playing audio as input. An audio amplifier was connected to the output. As the knob turned, we could clearly hear the difference in audible volume.

## Volume control

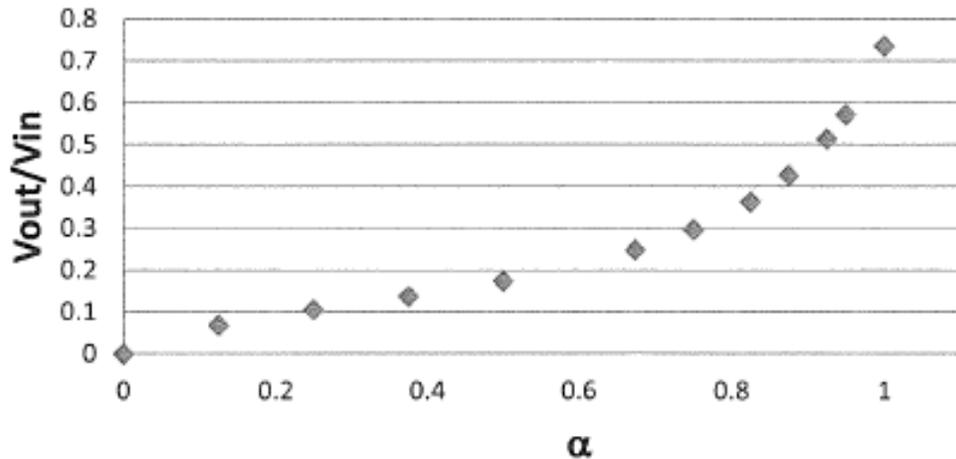

### Discussion:

In general, our circuit worked as expected. We see a fairly exponential increase in  $V_{out}/V_{in}$  vs.  $\alpha$ . Correspondingly, when our ear takes the logarithm, we get a linear increase in sound volume vs.  $\alpha$  as desired. Our results shown above, and our test-drive confirmed this.

There were some % differences in the actual circuit compared to what was predicted based on theory alone. This might be due to inaccurate measurement of  $\alpha$ . It might also be due to our voltage readings being a bit off.

The circuit might be better if we could achieve a larger  $V_{out}/V_{in}$  when the knob is turned all the way up so that we don't waste voltage in the circuit.

### Appendix:

The expression for  $V_{out}/V_{in}$  provided comes from a voltage divider equation:

$V_{out}/V_{in} = R_p/R_s + R_p$ , where  $R_s = R_1 + (1-\alpha)R_2$ , and  $1/R_p = 1/\alpha R_2 + 1/R_3$ .

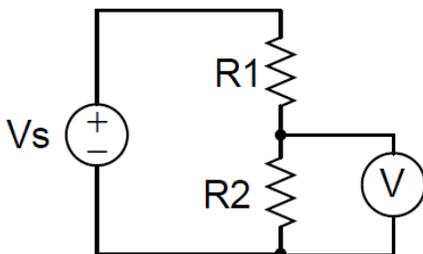


Figure 1. Basic voltage divider circuit

