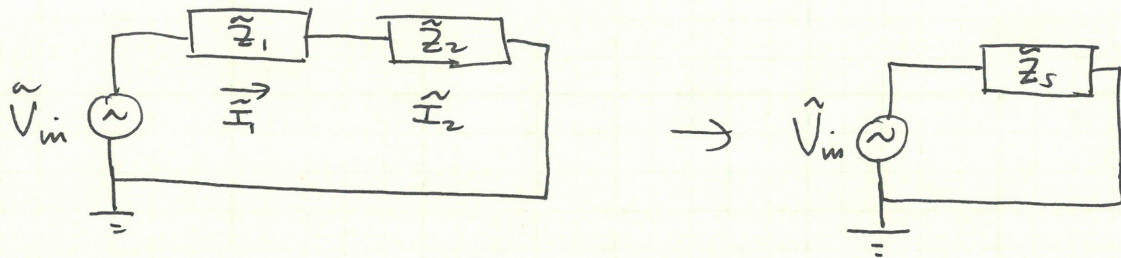


SERIES IMPEDANCE



$$V_{in}(t) = V_1(t) + V_2(t) \quad (1)$$

$$V_{in} \cos(\omega t + \phi_{in}) = V_1 \cos(\omega t + \phi_1) + V_2 \cos(\omega t + \phi_2) \quad (2)$$

$$\text{Re} \left[\underbrace{v_{in} e^{j\phi_{in}}}_{\tilde{V}_{in}} e^{j\omega t} = \underbrace{v_1 e^{j\phi_1}}_{\tilde{V}_1} e^{j\omega t} + \underbrace{v_2 e^{j\phi_2}}_{\tilde{V}_2} e^{j\omega t} \right] \quad (3)$$

$$\tilde{V}_{in} = \tilde{V}_1 + \tilde{V}_2 \quad (4)$$

$$= \tilde{I}_1 \tilde{Z}_1 + \tilde{I}_2 \tilde{Z}_2 \quad (5)$$

$$i_1(t) = i_2(t) \quad [\text{KCL}]$$

$$\therefore \tilde{I}_1 = \tilde{I}_2 = \tilde{I} \quad (6)$$

$$\tilde{V}_{in} = \tilde{I} (\underbrace{\tilde{Z}_1 + \tilde{Z}_2}_{\equiv \tilde{Z}_S}) \quad (7)$$

series equiv. impedance

$$\boxed{\tilde{Z}_S = \tilde{Z}_1 + \tilde{Z}_2} \quad (8)$$