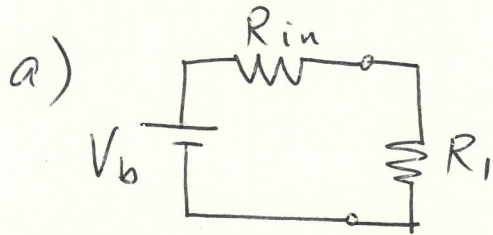


# COUNT FLAPOLA



$$R_{in} = 0.32 \Omega$$

$$V_b = 6V$$

$$R_1 = ? \quad (\text{see part b})$$

- b) motor current = 960 mA at full speed.  
= Total current flow in circuit in part a)


$$i_{max} = \frac{V_b}{R_{in} + R_1}$$

$$R_{in} + R_1 = \frac{6V}{960mA}$$

$$= 6.25 \Omega$$

$$R_1 = 6.25 \Omega - 0.32 \Omega = \boxed{5.93 \Omega}$$

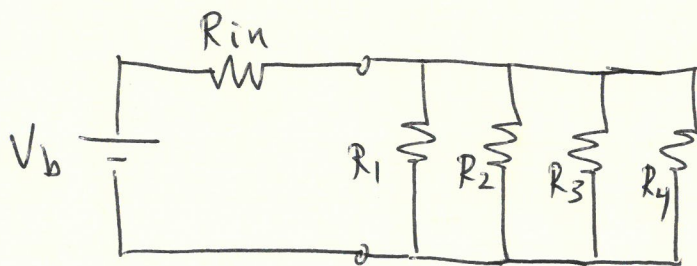- c) All motors plug in parallel to the battery.  
This connects all motors to the same two battery terminals




d)  $R_1 = R_2 = R_3 = R_4 = R_m = 5.93 \Omega$

These are all in parallel giving  
~~total~~ parallel equivalent  $R_p = \frac{5.93 \Omega}{4} = 1.4825 \Omega$

This can be easily computed using  $\frac{1}{R_p} = \sum \frac{1}{R_i}$

Or, more intuitively, there are 4 paths for current to flow, so the resistance is 4x less (conductance is 4x greater).

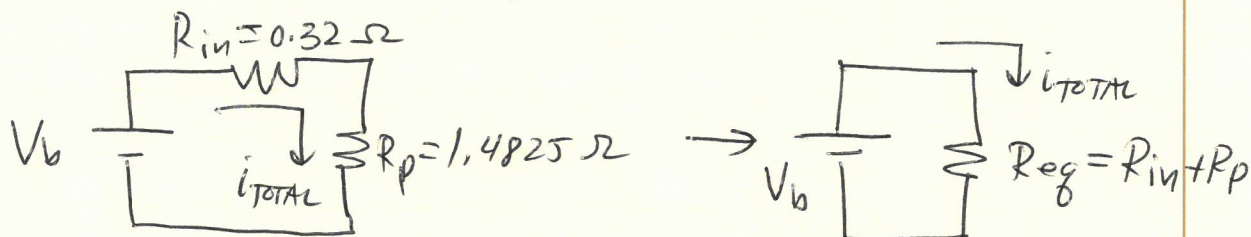
Now for total equiv resistance, we just add the battery internal resistance in series



$$R_{eq} = 1.4825 + 0.32 \Omega = \boxed{1.8025 \Omega}$$


e) The total current flow  $i_{TOTAL} = \frac{V_b}{R_{eq}} = \frac{6V}{1.8025 \Omega} = \underline{\underline{3.33 A}}$

Thus across  $R_{in}$  we have

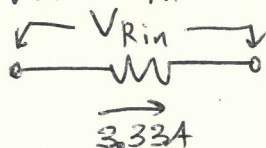

Ohm's Law  $\Rightarrow V_{R_{in}} = i_{TOTAL} R_{in}$   
 $= (3.33 A)(0.32 \Omega)$   
 $= \underline{\underline{1.065 V}}$

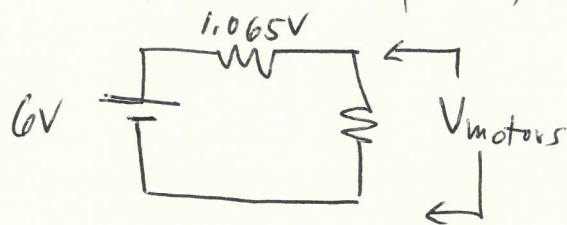e cont'd) For the 4 motors, we can use KVL to find that voltage drop is!



$$6V - 1.065V = V_{motors}$$

$$\underline{\underline{V_{motors} = 4.935V}}$$

The total current splits 4 ways, equally across all motors, since they are all the same motor:

$$i_{motor} = \frac{i_{TOTAL}}{4} = \underline{\underline{0.832A}}$$

f) Battery charge is  $q = 1600 \text{ mAh}$

$$i_{TOT} = \frac{\Delta q}{\Delta t} \quad \Delta t = \frac{\Delta q}{i_{TOT}} = \frac{1600 \text{ mAh}}{3.33A} = \underline{\underline{0.48 \text{ hr}}}$$

The motors can run for  $t = 0.48 \text{ hr} = \underline{\underline{28.8 \text{ min}}}$

g)  $P = i^2 R$

motors:  $P_{motors} = (i_{TOT})^2 (R_p)$

↑  
parallel equiv of all motors

$$= (3.33A)^2 (1.4825\Omega)$$

$$= 16.43 \text{ W}$$

battery:  $P_{battery} = (i_{TOT})^2 (R_{in})$

$$= (3.33A)^2 (0.32\Omega)$$


$$= 3.55 \text{ W}$$

$$\text{Ratio: } \frac{P_{motors}}{P_{battery}} = \frac{16.43}{3.55} = \underline{\underline{4.63}}$$

Note: We lose ~ 18% of power due to battery resistance



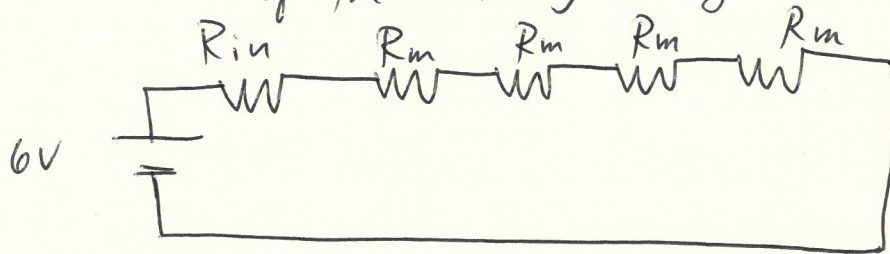h) Given 6V battery, note 1.5V is  $\approx \frac{1}{4}$  of this  
 What if the motors were connected  
in series, each motor dropping  $\approx \frac{1}{4}$   
 of the battery voltage?



$$\begin{aligned} \text{Total series resistance} &= R_{in} + 4R_m = R_s \\ &= 0.32 + 4(5.93 \Omega) \\ &= 24.04 \Omega \end{aligned}$$

Total current flow in this case:

$$i_{\text{TOTAL, SERIES}} = \frac{V_b}{R_s} = \frac{6V}{24.04 \Omega} \approx 0.25 A$$

Voltage drop across one motor

$$\begin{aligned} V_m &= i_{\text{TOTAL, SERIES}} R_m = (0.25 A)(5.93 \Omega) \\ &= \underline{\underline{1.48 V}} \end{aligned}$$

This substantiates the claim about miswiring  
 was putting motors in series