

Pump up the Jam: DIY Audio Amp (CBL Module #4, fall 2022)

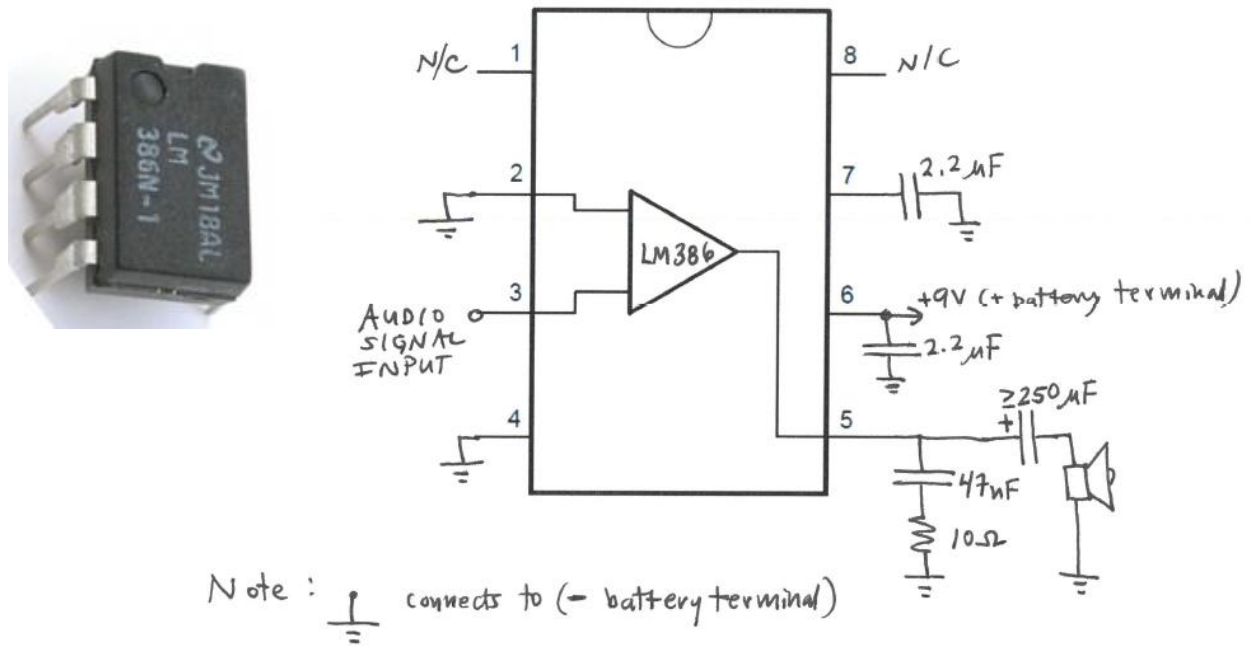


Figure 1. LM386 audio amplifier wiring. Remember to properly orient the op-amp - look for the little dot or half-moon orientation mark on the IC package. You can easily add a slick little volume control using a potentiometer (see figure 3)!

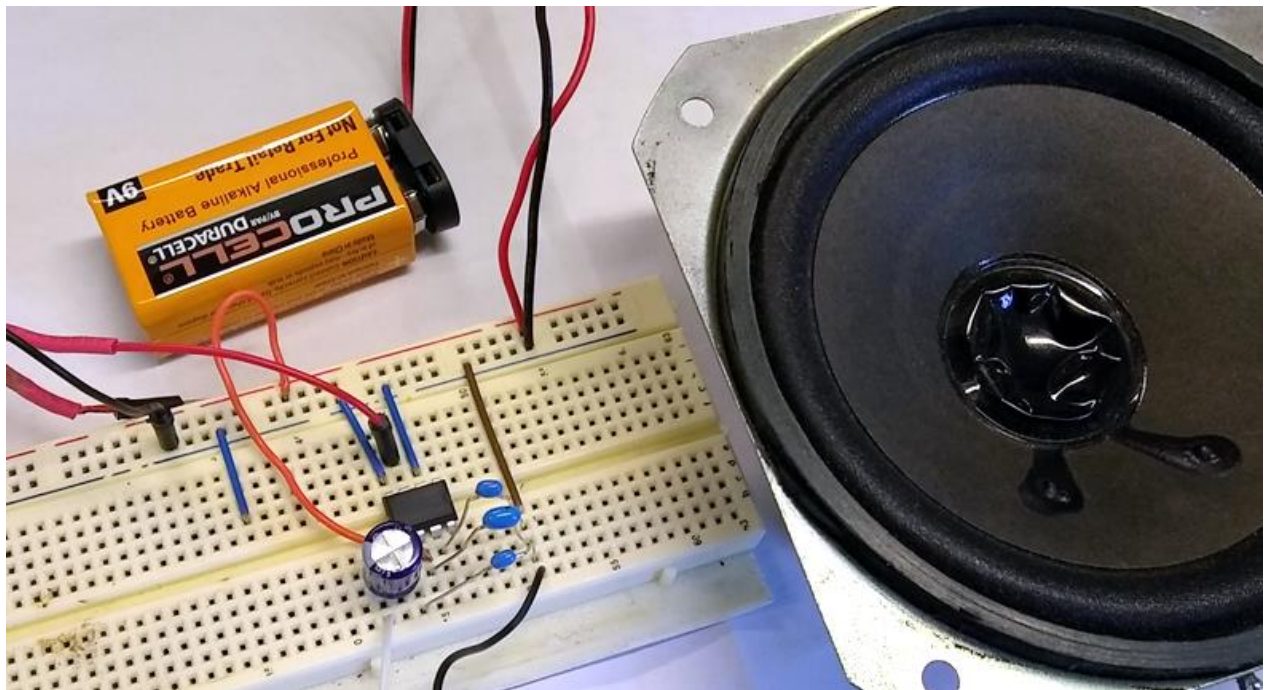


Figure 2. Implementation of the LM386 Audio Amplifier. Note the wiring: nice, tight, simple.

The circuit schematic below shows an optional volume control. It's really easy to implement using a 10k pot (as a voltage divider!!)

9.2.1 LM386 with Gain = 20

Figure 10 shows the minimum part count application that can be implemented using LM386. Its gain is internally set to 20.

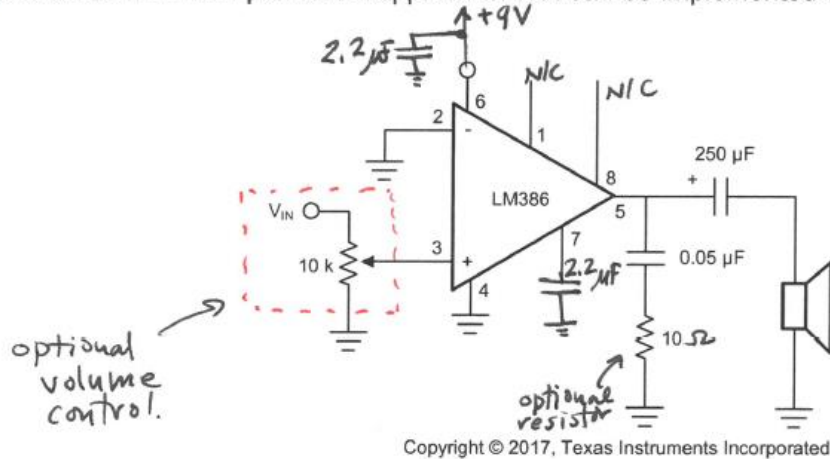


Figure 10. LM386 with Gain = 20

Figure 3. Circuit schematic of LM386 amplifier. Image adapted from TI LM386 datasheet.

An amplifier takes a small signal and makes it bigger! Today's smart phones only output a fraction of a volt, just not enough to drive a speaker. Hence, why we need to amplify the audio signal before playing it through the speaker. Today we'll build a classic audio amp based around the classic TI LM386. By virtue of internal construction, It is set for a gain of 20. This means if you put a 0.1 V amplitude sine wave in, you'll get a $20 \times 0.1 \text{ V} = 2.0 \text{ V}$ signal out. The sound quality is quite impressive. So let's build one!

Build notes:

- It should take about ≤ 20 min to construct the system by a relatively experienced hand.
- The LM386 amplifier is internally constructed to have a **gain = 20**.
- **The giant 250 uF capacitor is electrolytic—it is polarized. Make sure to orient it properly**, else it can blow up. Be sure to connect the positive terminal to the output of the amplifier.
- The entire system is **powered by a 9V battery**. This means the amplifier oscillates around a baseline of 4.5V Volts. Of course, only oscillations matter—we want sound *waves* after all! The giant 250 uF capacitor and the speaker is essentially form a **high pass filter**, cutting out the 4.5V offset, letting just the oscillating waves pass. Those waves are the sound we want to hear!
- The 2.2 uF capacitors are called "**bypass capacitors**". They help maintain a constant 9V supply to the amplifier even when its power demands vary in time. For instance, if a big bass boom comes through, that requires a lot of power. The battery might not be able to deliver enough

current all at once. The capacitors release some of their stored charge to help the battery in a time of need!

- The 47 nF capacitor connected to the output acts like a **short circuit for high frequency noise**, essentially filtering it out. The 10 ohm resistor can be something a little larger, or many a builder has found it can be just short circuited (0 Ohms).

Volume Control:

Add a volume control to your system! All you need is a single potentiometer. As you turn the knob the volume increases or decreases accordingly. Add one to your system, as indicated in figure 3

How does this work? The + terminal of the amplifier sees the voltage across the 'bottom' of the potentiometer. Volume is maximum when the wiper is at the top (connected straight to the audio source; maximal resistance in pot); and minimal when the wiper is at the bottom (shorted ground; minimum resistance in bottom of pot).

One really fun thing to do is view the audio signals in real time using a mobile device oscilloscope app. I like "Sound Oscilloscope" by Bolden in the Google Play store. I imagine there is something similar for iPhone and/or laptops.