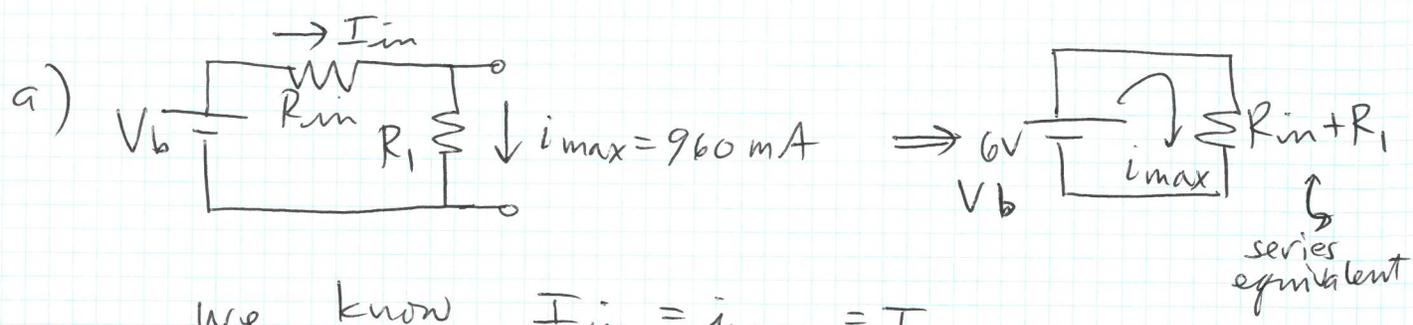


COUNT FLAPULA




We know $I_{in} = i_{max} = I$

Ohm's Law : $i_{max} = \frac{V_b}{R_{in} + R_1}$

$\Rightarrow R_{in} + R_1 = \frac{V_b}{i_{max}} = \frac{6V}{960mA} = 6.25 \Omega$

$R_1 = 6.25 \Omega - 0.32 \Omega = \boxed{5.93 \Omega}$


This is the resistance of a motor.

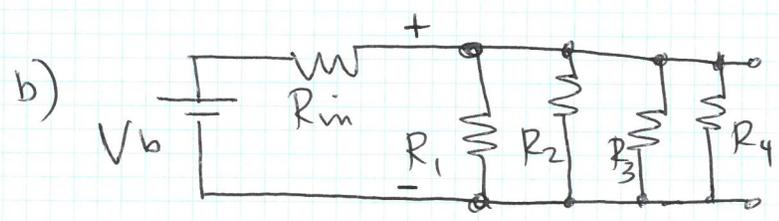

~~This~~ This configuration, all 4 motors plug directly into the power supply (NiMH battery). Think about the + and - terminals of the battery and where they line on the diagram.

One common idea/question is "How about series config?"

Try it!

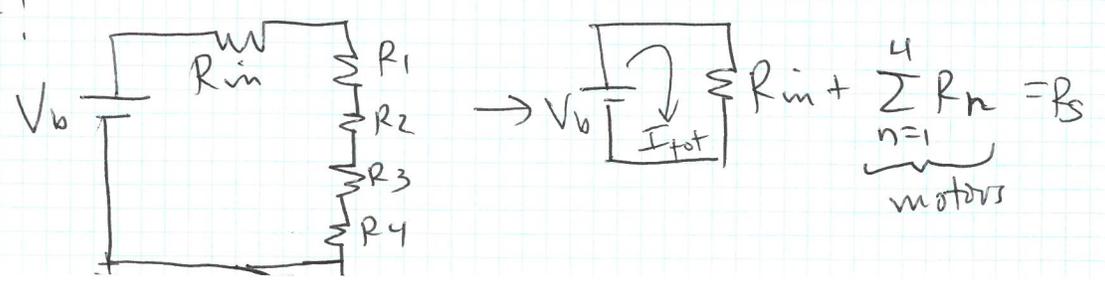


$$I_{tot} = \frac{V_b}{R_s} \leftarrow 6V$$

$$R_s \leftarrow 0.32 + 4(5.93\Omega) \approx 24\Omega$$




(2)

Thus $I_{tot} \approx \frac{6V}{24\Omega} = \frac{1}{4} A$

For one motor, example R_1

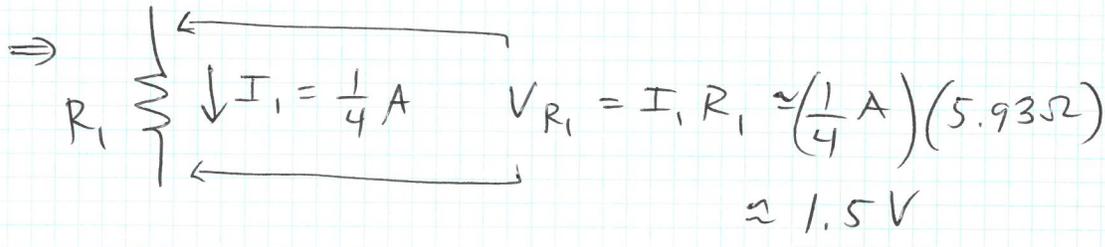

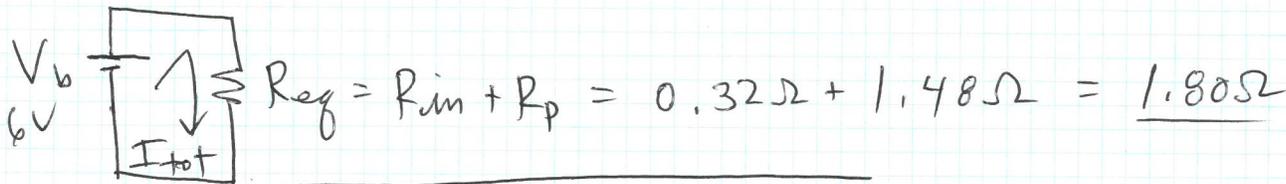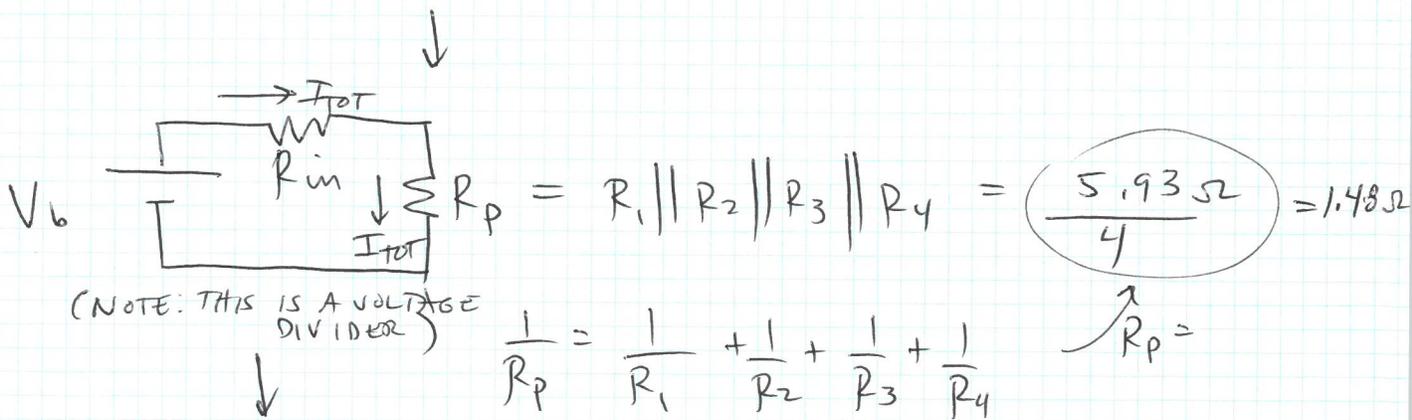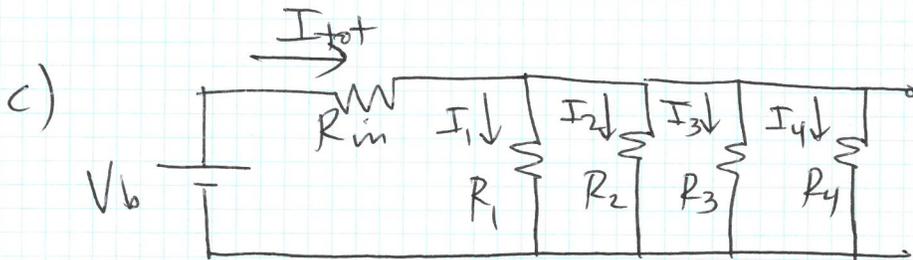Uh-oh, this won't work, voltage supplied is too low! (see part f).




$$I_{tot} = \frac{6V}{1.8\Omega} = 3.3 A \quad (3)$$

current splits equally 4 ways in motors - they are identical:

$$I_1 = I_2 = I_3 = I_4 = \frac{1}{4} I_{TOT} = 833 mA \quad (4)$$

voltage dropped internally in battery

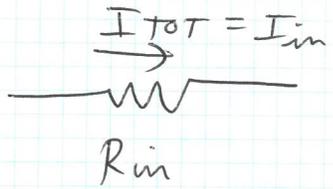

$$V_{in} = I_{in} R_{in} = I_{TOT} R_{in}$$

$$= (3.33A)(0.32\Omega)$$

$$V_{in} = \underline{\underline{1.06V}} \quad (2)$$

voltage dropped across motors: KVL:



$$V_b = V_{in} + V_{motors}$$


$$V_{motors} = V_b - V_{in}$$

$$= 6V - 1.06V$$

$$V_{motors} = \underline{\underline{4.94V}}$$

↑ same voltage across all; they are in parallel!

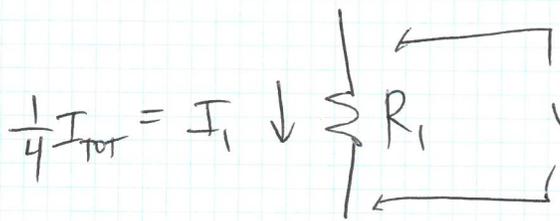Alternatively / equivalently, apply Ohm's Law




$$V_{R1} = I_1 R_1 = \left(\frac{I_{TOT}}{4}\right) R_1$$

$$= (833mA)(5.93\Omega)$$

$$= \underline{\underline{4.94V}}$$

-OR- invoke voltage divider:

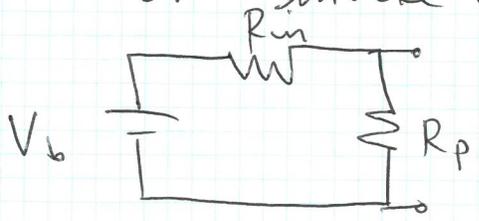

$$V_{Rp} = V_b \left(\frac{R_p}{R_{in} + R_p} \right) = \frac{R_1}{4}$$


you will get the same answer

d) We computed in part c) that $I_{TOT} = 3.33A$. (4)

The battery has $1600 \text{ mAh} = 1.6 \text{ A} \cdot \text{hr}$

$$\text{Thus } \Delta t = \frac{1.6 \text{ A hr}}{3.33 \text{ A}} \approx \boxed{29 \text{ min}} \text{ or } \approx \frac{1}{2} \text{ hr}$$

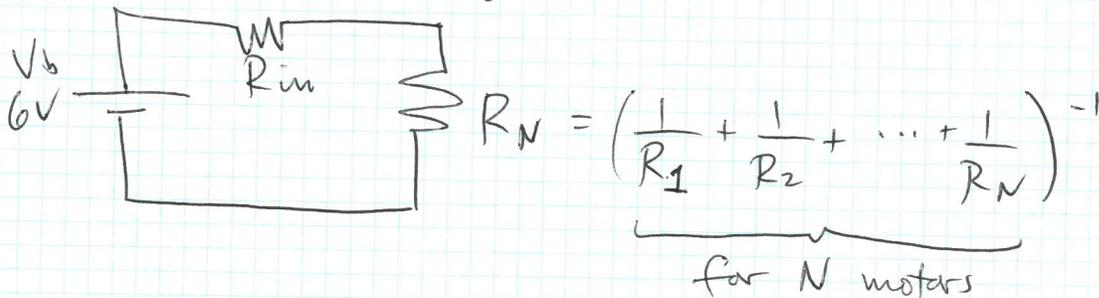e) Note we're already on the hairy edge with 4 motors powered at $4.94V$, so intuitively we don't expect many more one possible to add before dropping below the $4.8V$ cutoff.



$$R_N = \frac{R_1}{N}$$

Voltage across motors is V_{RN} .

$$\begin{array}{ccc} V_{RN} = V_b \left(\frac{R_N}{R_{in} + R_N} \right) & \text{solve } R_N. \\ \uparrow & \uparrow \\ \text{set to} & 6V \\ 4.8V & \uparrow \\ & 0.32\Omega \end{array}$$

$$V_{RN} (R_{in} + R_N) = V_b R_N \Rightarrow \cancel{V_{RN} R_{in}} + \cancel{V_{RN} R_N} = V_b R_N$$

$$V_{RN} R_{in} + V_{RN} R_N = V_b R_N \Rightarrow R_N = \frac{V_{RN} R_{in}}{(V_b - V_{RN})} = \frac{(4.8V)(0.32\Omega)}{(6 - 4.8)V}$$

(5)

$$R_N = 4 (0.32 \Omega) = 1.28 \Omega.$$

$$\begin{aligned} \text{Recall } R_N &= \frac{R_1}{N} \Rightarrow N = \frac{R_1}{R_N} = \frac{5.93 \Omega}{1.28 \Omega} \\ &= \underline{\underline{4.63 \text{ motors}}} \end{aligned}$$


Of course we have to have integer number of motors, so 4 is the max

[This is a tricky part of the problem - but achievable]

f) They were wired in series! See page (2)

SOIL MOISTURE MONITOR


①

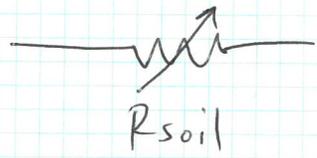

This is a variable resistor depending on hydration of soil.

Need to add more elements to sense a change in resistance

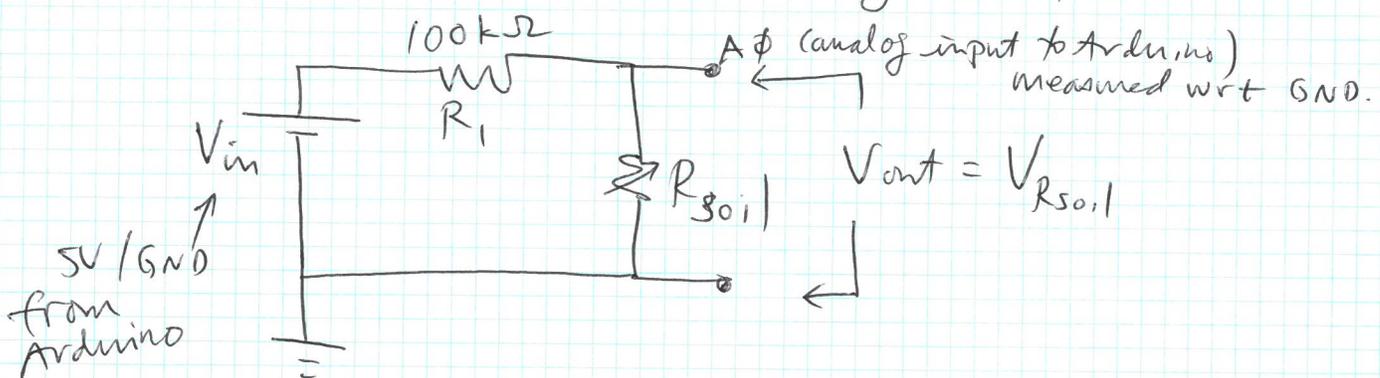This is just like our CDS photocell lab so we can do something like this:



Measure output across R_{soil}
Need to choose R_1 sensibly.

$$V_{out} = V_{R_{soil}} = V_{in} \left(\frac{R_{soil}}{R_1 + R_{soil}} \right)$$

VOLTAGE DIVIDER! NOTE: THIS IS JUST OHM'S LAW IN HIDING : $I_1 = I_{R_{soil}} = \frac{V_{in}}{R_1 + R_{soil}}$


We know R_{soil} ranges from $\approx 30 - 300 k\Omega$.

Choose $R_1 \approx 100 k\Omega$ in middle of this range for R_{soil}
What, then, is expected dynamic range wet vs. dry?

Wet : $R_{soil} \approx 30k\Omega \Rightarrow V_{out} \approx 6V \left(\frac{30k\Omega}{130k\Omega} \right) = 1.38V$

dry : $R_{soil} \approx 300k\Omega \Rightarrow V_{out} \approx 6V \left(\frac{300k\Omega}{400k\Omega} \right) = 4.5V$

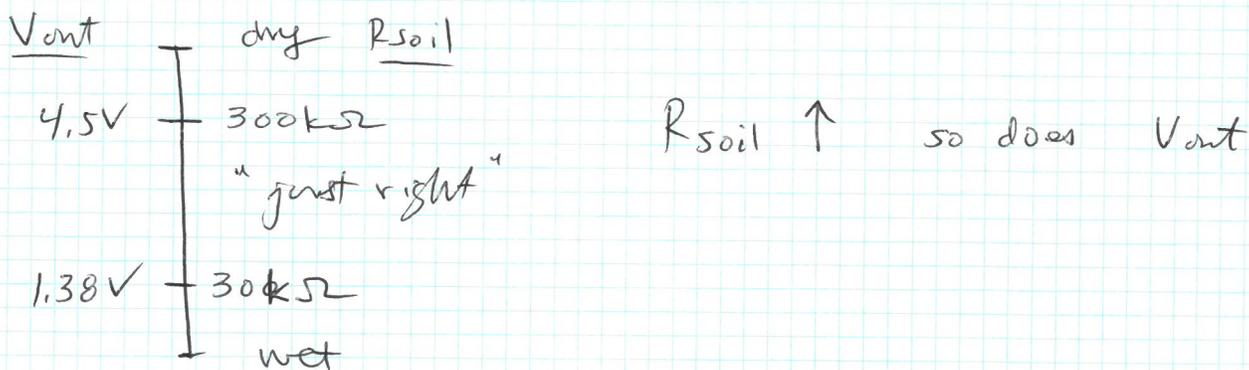That's a nice big change from 1.38 to 4.5V
(at bare minimum!) wet vs. dry.



```

Arduino code : int sensorVal = analogRead(A0);
                float Vout = sensorVal (5.0/1023);
if (Vout < 1.38) {
    digitalWrite(greengreenpin, HIGH);
    digitalWrite(yellowpin, LOW);
    digitalWrite(redpin, LOW);
}

```

```

else if (Vout > 4.5) {

```

```

    pseudocode // greenpin → write LOW
    (I got lazy yellowpin → write LOW
    :)         redpin → write HIGH
    )
}

```

```

else { // just rightright (write"? )


```

```

    green → LOW
    red → LOW
    yellow → HIGH
}

```

LED CIRCUITRY

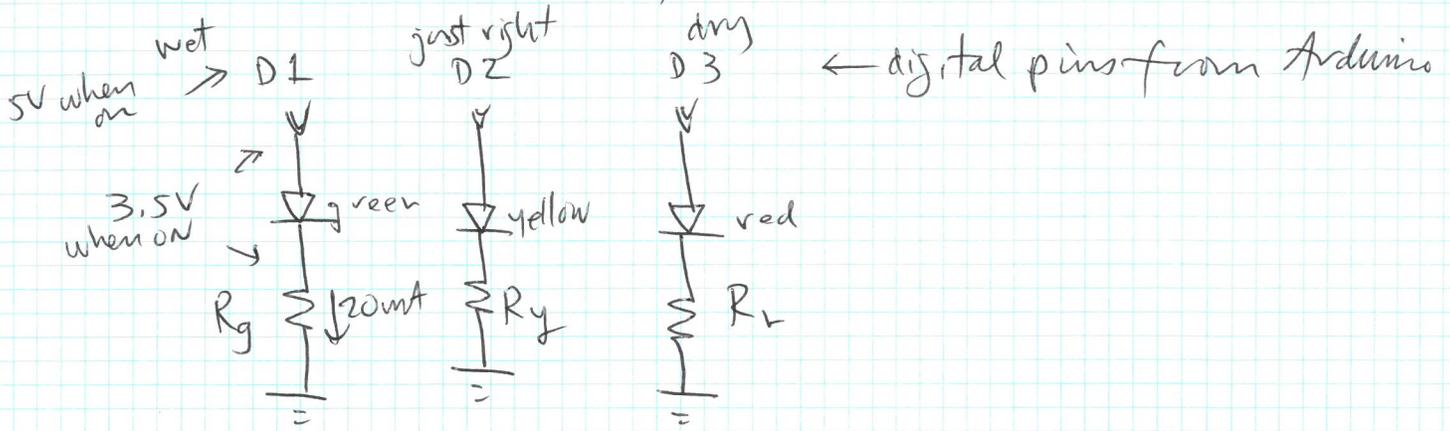

For example calc of choosing current limiting resistor.


GREEN : green turn on voltage is $\approx 3.5V$ (from table provided)

If LED illuminated: $D_1 = 5V$ w/AT ground.

LED eats up 3.5V so 1.5V must drop across R_g (KVL). Formally.

$$5V = \underbrace{V_{LED}}_{3.5} + \underbrace{V_{R_g}}_{1.5V}$$

$$V_{R_g} = 1.5V = I_{R_g} R_g$$

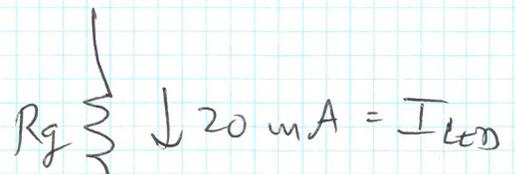

$I_{R_g} = 20mA$. all current flow through LED must flow R_g . It is a series combo LED- R_g !

$$\therefore R_g = \frac{1.5V}{20mA} = \underline{\underline{75\Omega}}$$

Compute similarly for yellow and red.