
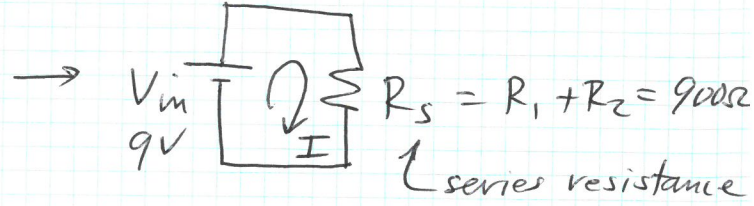


SOLUTIONS


①

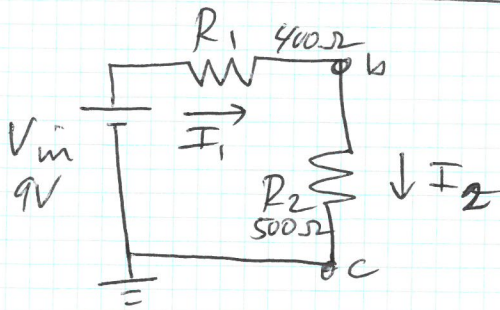

a) We know $I_1 = I_2 = I$ (take KCL @ ~~node a~~ @ node b)

$$I = \frac{V_{in}}{R_s} = \frac{9V}{900\Omega} = 0.1 A = \boxed{10 \text{ mA}}$$

b)

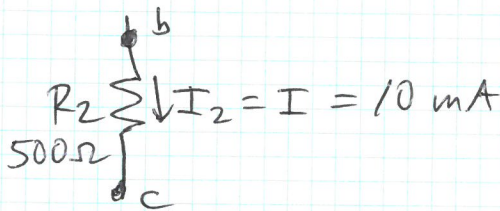


Ohm's Law

$$V_b - V_c = V_{R2} \stackrel{\text{by definition}}{=} I_2 R_2 = I R_2$$

$$V_{R2} = (10 \text{ mA})(500\Omega) = \boxed{5V}$$

c)

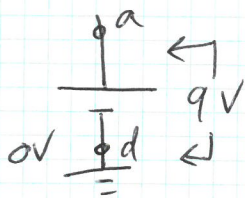

node d = ground (This is just a reference point to which we assign 0V)

node a is $\boxed{9V}$ higher than node d.

It's just the battery's voltage

d)

$$I = \frac{dq}{dt} \Rightarrow dt = \frac{dq}{I}$$

Δ time Δ charge capacity



$dq = 1000 \text{ mA hr}$ to fully drain battery

$$dt = \frac{1000 \text{ mA hr}}{10 \text{ mA}} = \boxed{100 \text{ hr}}$$

e)

"VOLTAGE DIVIDER" or "SERIES CIRCUIT"

2

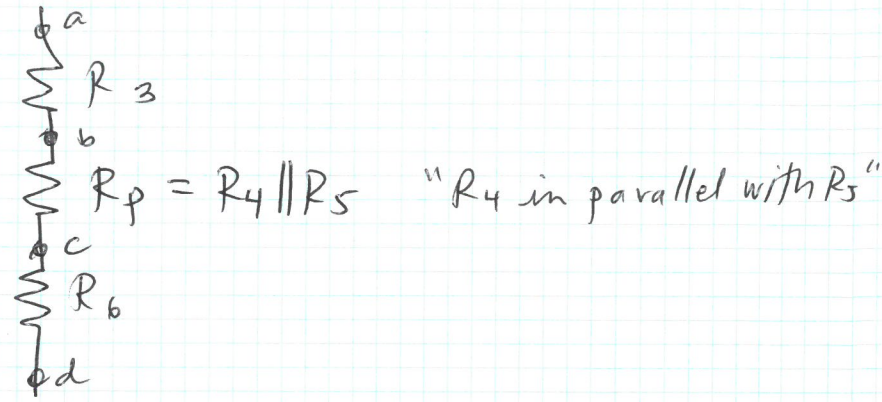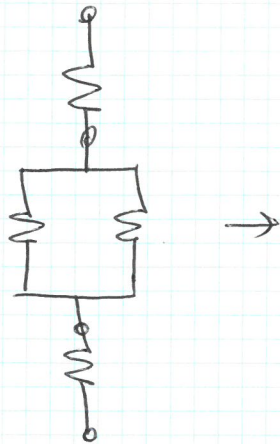


$$\frac{1}{R_p} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{100\Omega} + \frac{1}{100\Omega} = \frac{2}{100\Omega}$$

$$\Rightarrow \boxed{R_p = 50\Omega} \quad \text{Note that this is } \frac{1}{2} \times 100\Omega$$

Two equal resistance paths in parallel halves the equivalent resistance

Then just add in series

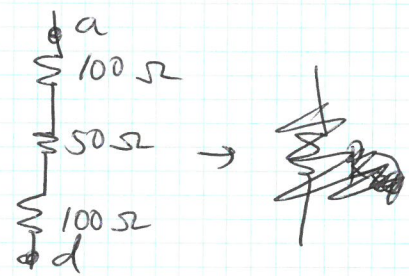

$$\boxed{R_{eq} = 250\Omega} \quad 100\Omega + 50\Omega + 100\Omega$$

b) Decrease

adding resistors in parallel always decreases the equivalent resistance

(series always increases)

③

$$\begin{array}{cccccccc} 1 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \\ \hline & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ 128 & | & 64 & | & 32 & | & 16 & | & 8 & | & 4 & | & 2 & | & 1 & | \end{array}$$

$$= 128 + 8 + 4 + 2 + 1$$

$$= 128 + 15 = \underline{\underline{143}}$$