

Two quick experiments to get up and running with Picoscope: Circuits fall 2022

(compiled JE 19 Oct 2022).

1. Generate and directly measure sine wave
2. Voltage divider example. Drive divider with sine wave from AWG. Measure V_{in} and V_{out} on channels A and B to visualize relationship thereof.



Figure 1. Connections for Generating a waveform and measuring it directly. The output waveform (AWG) is connected directly to input chan A with a coax cable. The picoscope is connected to the laptop via USB.

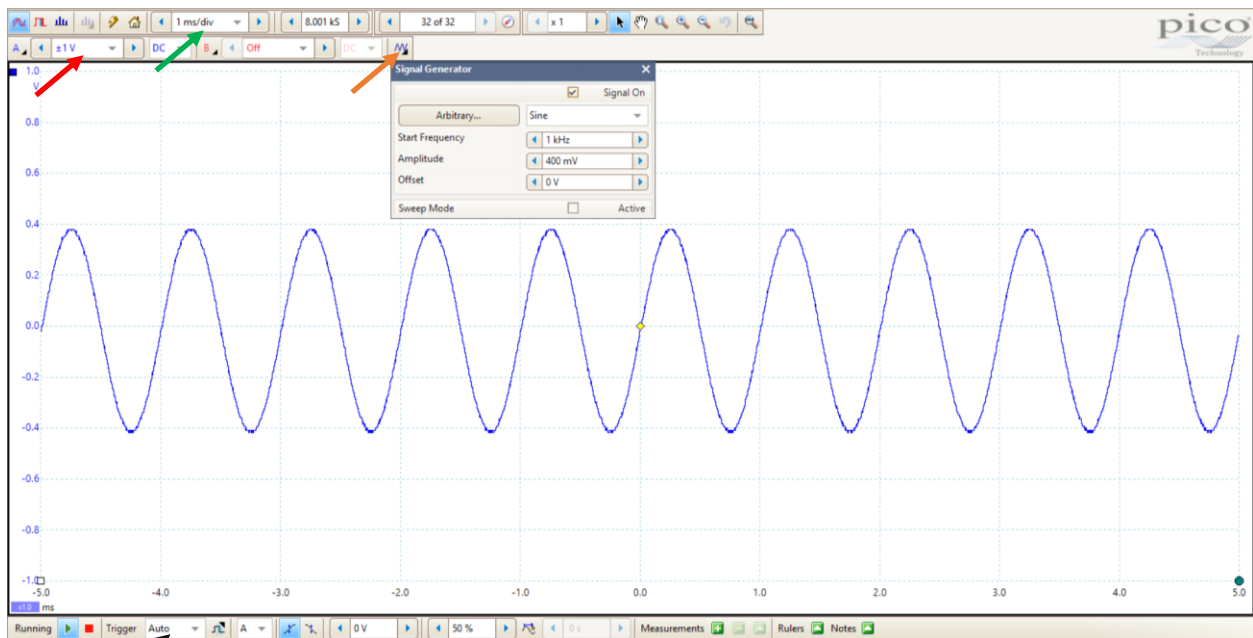


Figure 2. Basic controls on picoscope. Orange arrow: configure waveform generation. Remember to check the box Signal On to actually generate the wave! Green arrow: set timebase. 1 'div' (division) is one dotted box worth of time. 1 ms/div makes sense here because it is well-matched at the 1 kHz frequency wave being generated. Red arrow: adjust voltage scale. Black arrow: trigger settings help stabilize the phase of wave at which plot is generated. 'Auto' generally works well.

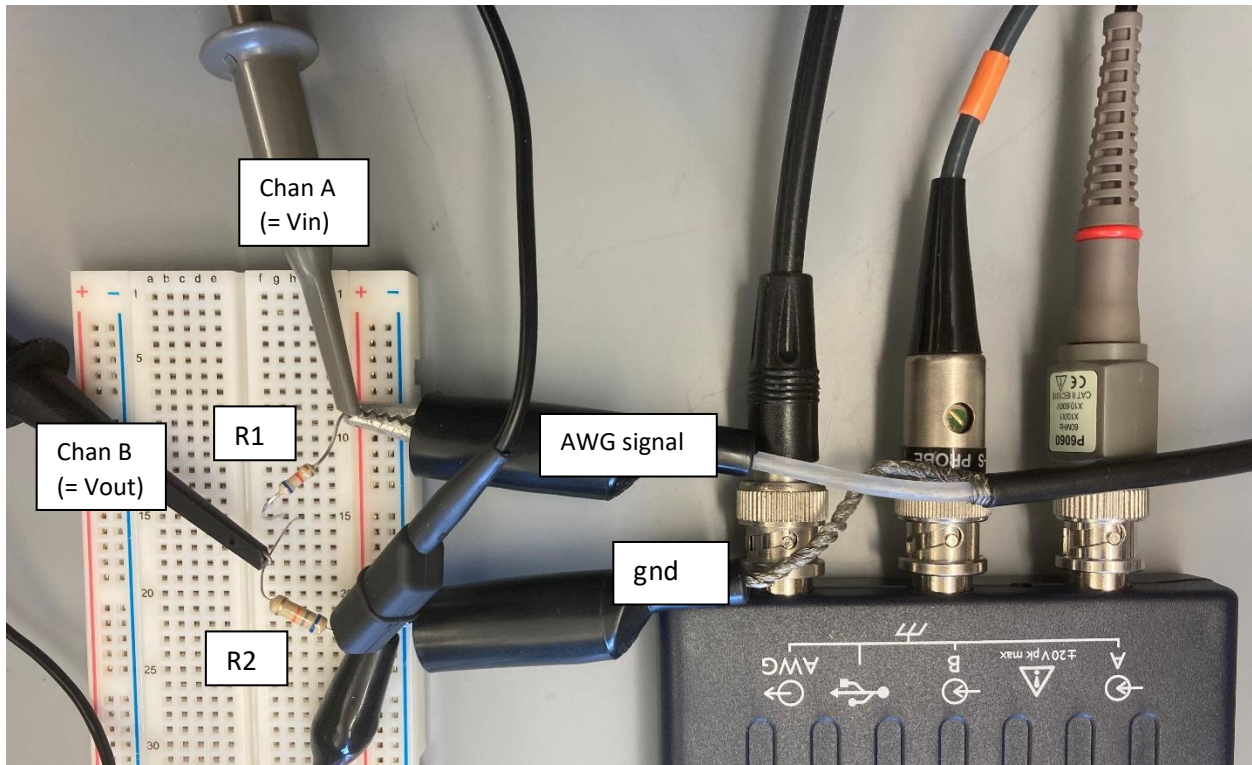


Figure 3. Typical connections for generating a wave, measuring input-output relationship. Voltage divider (68k and 68k) on breadboard. Note the ground clips all contacting the 'bottom' leg of R2. AWG is configured to generate a sine wave at desired amplitude and frequency. Connection is made to the voltage divider via a coax-to-alligator clip cable. Standard coax probe cables are used to measure inputs A and B.

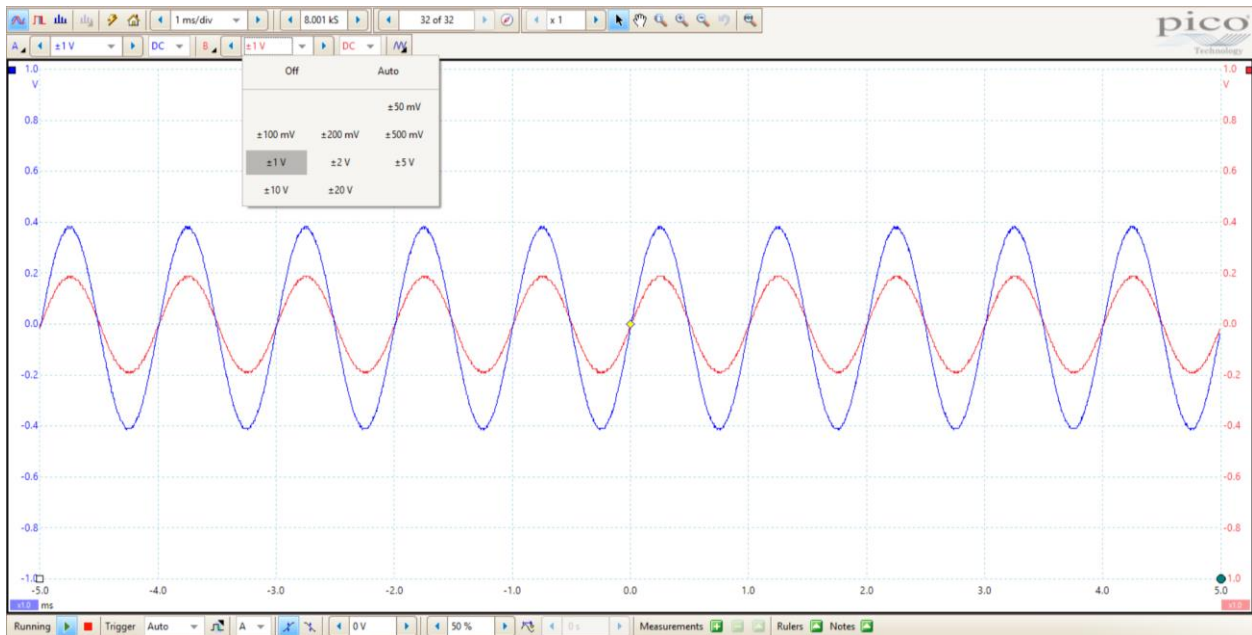


Figure 4. Visualizing two waves simultaneously, chan A (blue) and chan B (red). Remember to turn on channel B to visualize the wave (default is typically 'off'). Note the voltage division in action ($V_{out} = \frac{1}{2} V_{in}$, in this case because we have 2x 68k resistors)

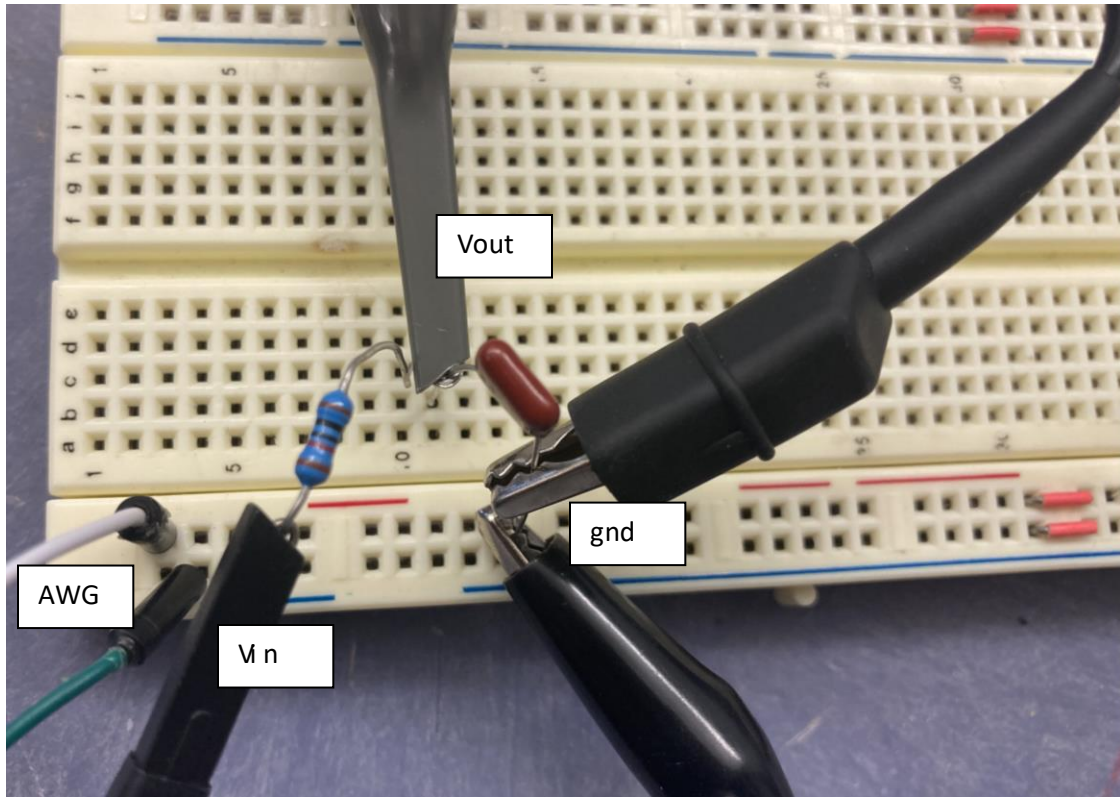


Figure 5. We can make the same V_{in} and V_{out} measurements for RC filters!. This time AWG is interfaced using 'quick connect' wires (white = signal wire connected to red power rail; green = GND on blue power rail). Note, this is a 1-stage LPF above.